

**avstdac.v (DAC Module)** The dac module converts the 10-bit digital signal from the rvmyth core to an analog output.

[avstdac]([https://github.com/vsdip/rvmyth\\_avstdac\\_interface.git](https://github.com/vsdip/rvmyth_avstdac_interface.git))

Inputs:

- D: A 10-bit digital input from the processor.
- VREFH: Reference voltage for the DAC.

Output:

- OUT: Analog output signal.

## Testbench

The testbench.v file is a test module to verify the functionality of vsdbabysoc. It includes signal initialization, clock generation, and waveform dumping for both pre-synthesis and post-synthesis simulations. Waveform Output:

- pre\_synth\_sim.vcd or post\_synth\_sim.vcd files generated based on simulation conditions.

## Simulation Steps

### Pre-Synthesis Simulation

Run the following command to perform a pre-synthesis simulation:


```
iverilog -o output/pre_synth_sim/pre_synth_sim.out -DPRE_SYNTH_SIM \
```

```
-I src/include -I src/module \
```

```
src/module/testbench.v src/module/vsdbabysoc.v
```

```
cd output/pre_synth_sim
```

```
./pre_synth_sim.out
```

 

```

module avsdac (
    OUT,
    D,
    VREFH,
    VREFL
);

    output OUT;
    input [9:0] D;
    input VREFH;
    input VREFL;

    reg real OUT;
    wire real VREFL;
    wire real VREFH;

    real NaN;
    wire EN;

    wire [10:0] Dext; // unsigned extended

    assign Dext = {1'b0, D};
    assign EN = 1;

    initial begin
        NaN = 0.0 / 0.0;
        if (EN == 1'b0) begin
            OUT <= 0.0;
        end
        else if (VREFH == NaN) begin
            OUT <= NaN;
        end
        else if (VREFL == NaN) begin
            OUT <= NaN;
        end
        else if (EN == 1'b1) begin
            OUT <= VREFL + ($itor(Dext) / 1023.0) * (VREFH - VREFL);
        end
        else begin
            OUT <= NaN;
        end
    end

    always @(D or EN or VREFH or VREFL) begin
        if (EN == 1'b0) begin
            OUT <= 0.0;
        end
        else if (VREFH == NaN) begin
            OUT <= NaN;
        end
        else if (VREFL == NaN) begin
            OUT <= NaN;
        end
        else if (EN == 1'b1) begin
            OUT <= VREFL + ($itor(Dext) / 1023.0) * (VREFH - VREFL);
        end
        else begin
            OUT <= NaN;
        end
    end
endmodule

```